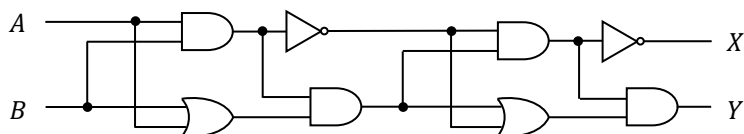


問14 図に示す論理回路の真理値表として、正しいものを次の(1)～(5)のうちから一つ選べ。



(1)

A	B	X	Y
0	0	1	0
0	1	1	0
1	0	1	0
1	1	1	0

(2)

A	B	X	Y
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

(3)

A	B	X	Y
0	0	1	1
0	1	1	0
1	0	0	1
1	1	1	0

(4)

A	B	X	Y
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	0

(5)

A	B	X	Y
0	0	1	0
0	1	0	1
1	0	1	0
1	1	0	1